



---

# Op-Amp applications

---

**By**

K.Akhil - EE24BTECH11035  
K.Teja Vardhan - EE24BTECH11034

2025-12-18

## Contents

<b>1</b>	<b>About LM358 ic</b>	<b>1</b>
<b>2</b>	<b>Custom Weighted Summing Amplifier</b>	<b>1</b>
<b>3</b>	<b>Op-Amp Integrator</b>	<b>1</b>
<b>4</b>	<b>Precision Rectifier (Super Diode)</b>	<b>1</b>

## 1 About LM358 ic


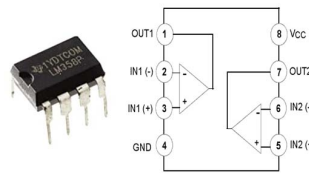


Figure 1: Schematic Diagram

The LM358 is a dual operational amplifier (op-amp) IC widely used in various analog electronic applications. It contains two independent, high-gain, internally compensated op-amps, which can be used for a wide range of tasks, such as signal amplification, filtering, and feedback control. The LM358 operates with a single supply voltage, typically ranging from 3V to 32V, making it suitable for low-voltage circuits. Due to its low power consumption and versatile application in both inverting and non-inverting configurations, the LM358 is a popular choice for many analog signal processing tasks.

## 2 Custom Weighted Summing Amplifier

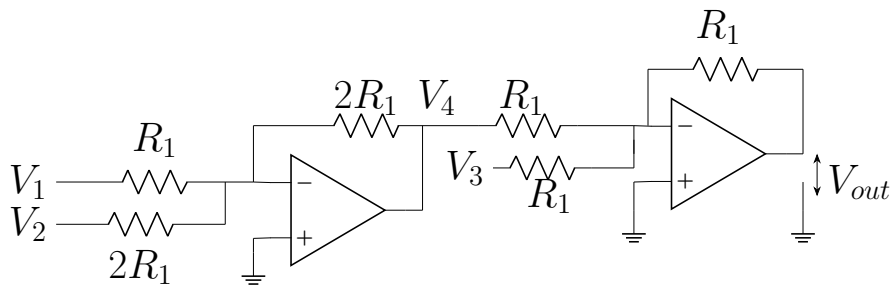

### Theory

- A **summing amplifier** is an op-amp circuit that combines multiple input signals into a single output signal. The output is a weighted sum of the input signals.
- The **inverting summing amplifier** uses an op-amp with multiple input resistors and a feedback

resistor. The output voltage is given by:

$$V_{\text{out}} = - \left( \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

where  $R_f$  is the feedback resistor, and  $R_1, R_2, R_3$  are the input resistors.

- By carefully selecting the resistor values, you can achieve specific weighting coefficients for the inputs. For example, to implement  $V_{\text{out}} = 2V_1 + V_2 - V_3$ , you would choose resistor values such that:

$$\frac{R_f}{R_1} = 2, \quad \frac{R_f}{R_2} = 1, \quad \frac{R_f}{R_3} = 1$$

- If a **non-inverting input** is required, you can combine inverting and non-inverting amplifiers.

## How to Perform the Experiment

- **Components Required:**

- Op-amp (e.g., LM358, TL081)
- Resistors (carefully selected for weighting)
- DC power supply
- Function generator (for input signals)
- Oscilloscope

- **Steps:**

- Design the circuit using an inverting summing amplifier configuration.
- Choose resistor values  $R_1, R_2, R_3$ , and  $R_f$  to achieve the desired weighting coefficients.
- Connect the input signals  $V_1, V_2$ , and  $V_3$  to the input resistors.
- Connect the feedback resistor  $R_f$  between the output and the inverting input of the op-amp.
- Power the op-amp using the DC power supply.
- Use the oscilloscope to measure the output voltage  $V_{\text{out}}$  and verify that it matches the expected weighted sum of the inputs.

By the following the above steps , we get the output response.

1.  $V_{\text{out}} = 2V_1 + V_2 - V_3$ ,  
Values taken are,  $V_1 = 3, V_2 = 4, V_3 = 7$ ,  
Then  $V_{\text{out}} = 3$

2.  $V_{out} = 2V_1 - V_3$  (By keeping  $V_2 = 0$ )  
Now, for the values,  $V_1 = 2$ ,  $V_3 = 3$ ,  
 $V_{out}$  is  $1V$

**For Case-I:**

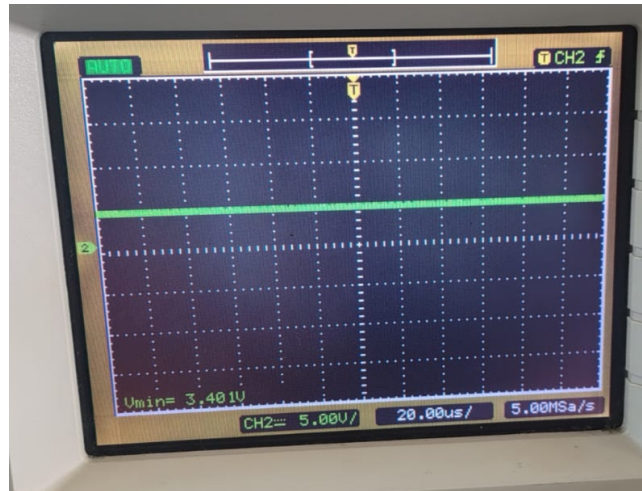


Figure 2: output

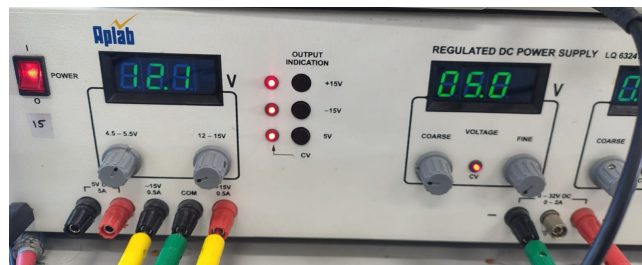


Figure 3: DC power supply

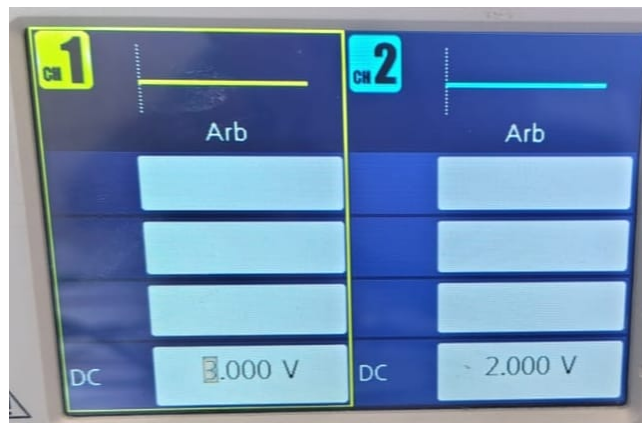


Figure 4: Function Generator

**Case-II:**

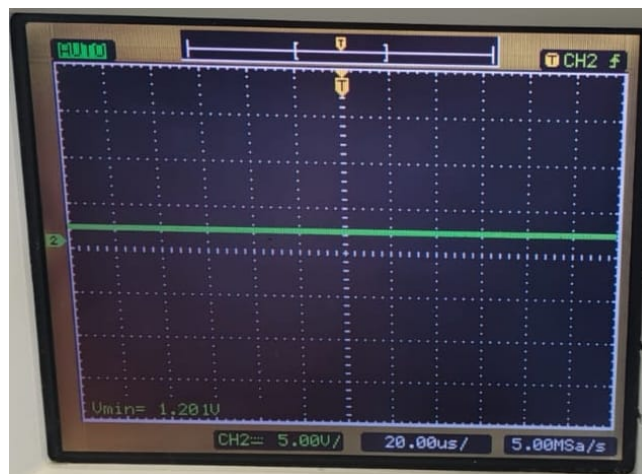


Figure 5: Output



Figure 6: Function generator


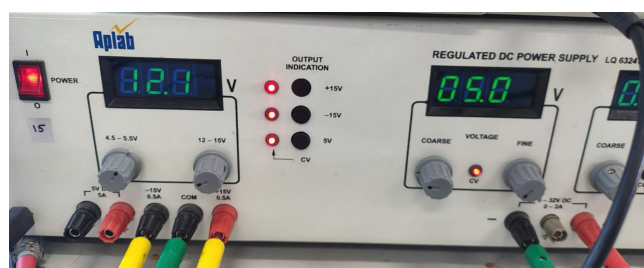


Figure 7: DC supply

### 3 Op-Amp Integrator

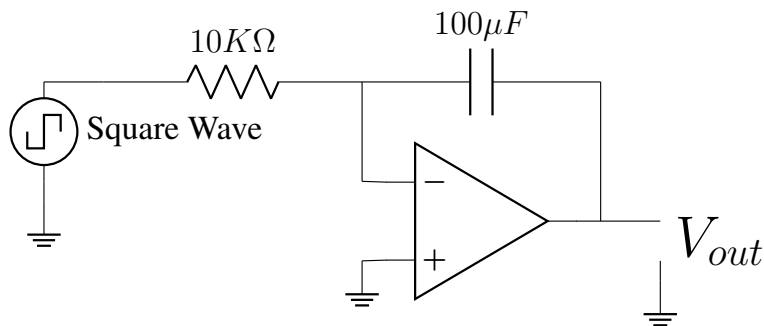

#### Theory

- An **op-amp integrator** performs mathematical integration of the input signal. The output voltage is proportional to the integral of the input voltage:

$$V_{out} = -\frac{1}{RC} \int V_{in} dt$$

where  $R$  is the input resistor, and  $C$  is the feedback capacitor.

- The integrator converts a **square wave input** into a **triangular wave output** because integration of a constant (square wave) results in a linear ramp (triangular wave).
- This circuit is widely used in signal processing, waveform generation, and control systems.

#### How to Perform the Experiment

- **Components Required:**
  - Op-amp (e.g., LM741, TL081)
  - Resistor ( $R$ )
  - Capacitor ( $C$ )
  - DC power supply
  - Function generator
  - Oscilloscope
- **Steps:**



- Design the integrator circuit by connecting the input resistor  $R$  to the inverting input of the op-amp and the feedback capacitor  $C$  between the output and the inverting input.
- Connect the non-inverting input of the op-amp to ground.
- Power the op-amp using the DC power supply.
- Apply a square wave input signal using the function generator.
- Use the oscilloscope to observe the output waveform. The output should be a triangular wave, confirming that the circuit is performing integration.


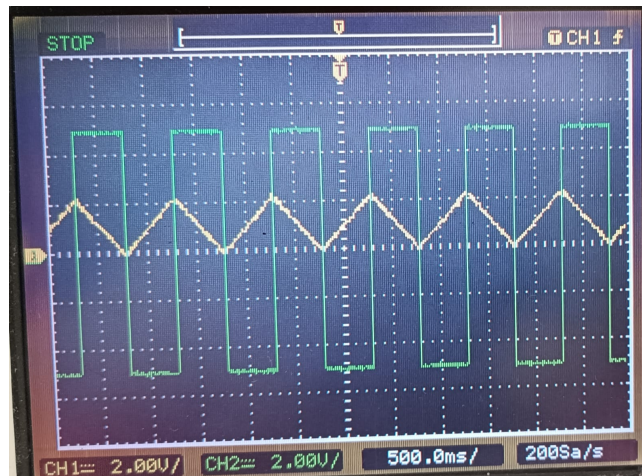


Figure 8: Op-Amp integrator when square input is given.

## 4 Precision Rectifier (Super Diode)

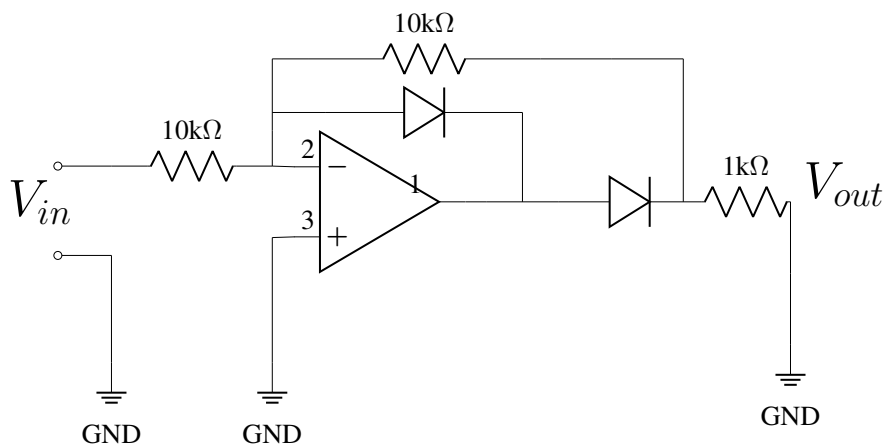

## Theory

- A **precision rectifier** uses an op-amp to eliminate the voltage drop (typically 0.7V) associated with a standard diode. This allows rectification of small AC signals with high accuracy.
- There are two types of precision rectifiers:
  - **Half-wave rectifier**: Passes only the positive half of the input signal.
  - **Full-wave rectifier**: Combines the positive half of the input signal with the inverted negative half, resulting in a fully rectified output.
- The op-amp ensures that the output follows the input without the diode's threshold voltage drop.

## How to Perform the Experiment

- **Components Required:**
  - Op-amp (e.g., LM358, TL081)
  - Diode (e.g., 1N4148)
  - Resistors
  - AC signal generator
  - Oscilloscope
- **Steps:**
- **Full-wave rectifier:**
  - Add an additional summing stage to combine the positive and inverted negative portions of the input signal.
  - Apply an AC input signal and observe the fully rectified output on the oscilloscope.

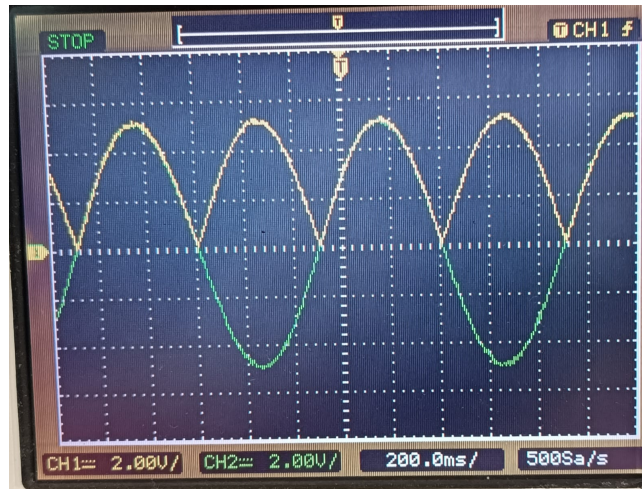


Figure 9: Full Wave rectifier.

## Summary of Steps for All Three Parts

- **Custom Weighted Summing & Difference Amplifier:**
  - Design the circuit with appropriate resistor values.
  - Apply input signals and measure the output to verify the weighted sum.
- **Op-Amp Integrator:**
  - Build the integrator circuit with a resistor and capacitor.
  - Apply a square wave input and observe the triangular wave output.
- **Precision Rectifier:**
  - Construct the half-wave or full-wave rectifier circuit.
  - Apply an AC input and observe the rectified output on the oscilloscope.